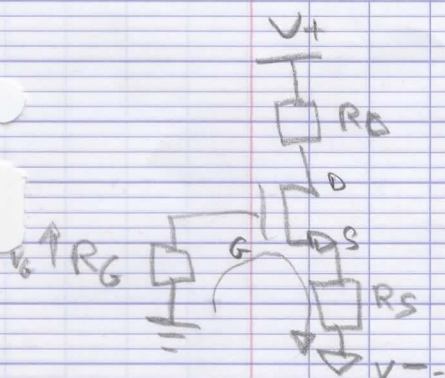


Rappel :
 $V_{th} = 1,3V$
 $\mu_n = 2 \text{ mA/V}^2$
 $\lambda = 0,02 \text{ V}^{-1}$

$$Z_C = \frac{1}{j\omega C} \rightarrow \begin{matrix} \omega=0 & Z_C = \infty \\ \omega=\infty & Z_C = 0 \end{matrix}$$

$$Z_L = j\omega L \rightarrow \begin{matrix} \omega=0 & Z_L = 0 \\ \omega=\infty & Z_L = \infty \end{matrix}$$

Q1) Schéma en DC :



$$I_G = 0A$$

$$R_G = 0$$

$$V_{OV} = V_{GS} - V_{th}$$

$$V_{GS} = V_{OV} + V_{th} = 1 + 1,3 = 2,3$$

Calculer RS :

$$V_G - V_{GS} - V_{RS} = V^-$$

$$-V_{RS} = V^- - V_G + V_{GS}$$

$$V_{RS} = -V^- + V_G - V_{GS}$$

$$R_S = \frac{-V^- + V_G - V_{GS}}{I_D}$$

$$R_S = \frac{15 + 0 - 2,3}{1 \cdot 10^{-3}} = 12,7 \text{ k}\Omega$$

$$Q2) \begin{cases} I_D = \frac{1}{2} \mu_n \frac{W}{L} \frac{(V_{GS} - V_{th})^2}{V_{OV}} \\ g_m = \frac{\partial I_D}{\partial V_{GS}} \end{cases}$$

$$g_m = \frac{\partial}{\partial V_{GS}} \frac{1}{2} \mu_n (V_{GS} - V_{th})^2$$

$$g_m = \frac{1}{2} \mu_n \cdot 2 (V_{GS} - V_{th}) = \mu_n (V_{GS} - V_{th})$$

$$\text{Maio } \mu_n = \frac{2 I_D}{(V_{GS} - V_{th})^2}$$

$$\text{Soit } g_m = \frac{2 I_D}{(V_{GS} - V_{th})} = \frac{2 I_D}{V_{OV}}$$

$$V_{GS} - V_{th} = \frac{2 I_D}{g_m} \Rightarrow V_{GS} = \frac{2 I_D}{g_m} + V_{th}$$

$$Q3 : r_o = \frac{1}{\lambda I_D} \text{ ou } r_o = \frac{V_A}{I_D}$$


$$V_{OV} = \sqrt{\frac{2 I_D}{\mu_n}} = 1V$$

$$g_m = \frac{2 \cdot 1 \cdot 10^{-3}}{1} = 2 \text{ mA/V}$$

$$r_o = \frac{1}{0,02 \cdot 1 \cdot 10^{-3}} = 50 \text{ k}\Omega$$


Signal AC

Modèle de Base

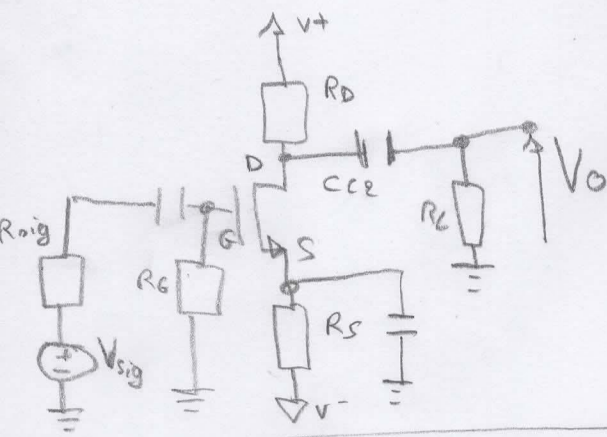


Petit signal

Q1

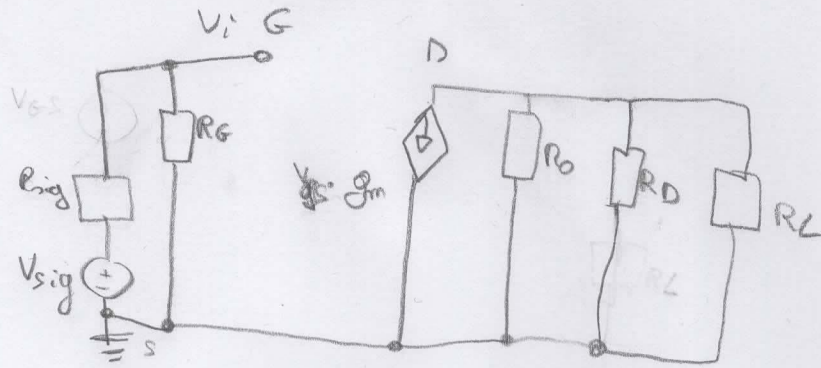

$$A_v = \frac{v_o}{v_i} = -g_m (R_D \parallel R_L \parallel R_o)$$

Q2)

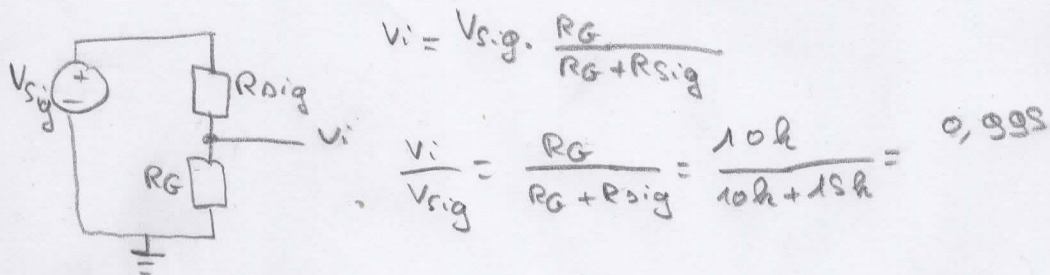

$$V_i = V_{sig} \cdot \frac{R_G}{R_G + R_{sig}}$$

$$\frac{V_i}{V_{sig}} = \frac{R_G}{R_G + R_{sig}} = \frac{10k}{10k + 15k} = 0,995$$

Q3) $R_{eq} = R_D \parallel R_L \parallel R_o = \frac{1}{\frac{1}{R_D} + \frac{1}{R_L} + \frac{1}{R_o}}$

$$A_v = -g_m \cdot R_{eq}$$

$$R_{eq} = \frac{A_v}{-g_m} = \frac{-2}{2 \cdot 10^{-3}} = -2,5k\Omega$$

Donc $\frac{1}{R_D} = \frac{1}{R_L} + \frac{1}{R_o} + \frac{1}{R_{eq}}$

$$\frac{1}{R_D} = 0,22 \Omega^{-1}$$

$$R_D = 3,52k\Omega$$

Q4) $V_D = V^+ - R_D \cdot I_D$
 $= 15 - 3,52 \cdot 10^3 \cdot 1 \cdot 10^{-3}$
 $= 11,43V$

Condition:

$$V_{DS} \geq V_{GS} - V_{th}$$

$$V_D \geq V_G - V_{th}$$

$$\downarrow \quad \downarrow$$

$$0V \quad 1,3V$$

Condition vérifiée